

# E4215 – Fall 2020

## Design Project: Programmable Anti-Aliasing Filter Design

Liping Hu, lh3009\* and Sinan Yilmaz, sy2943\*

\* Columbia University in the City of New York

**Abstract**—In this project, we designed an adjustable 6<sup>th</sup> order analog filter that is capable of performing six different filter responses, namely Butterworth Low-Pass Filter with 150 kHz cut-off frequency, Butterworth Low-Pass Filter with 300 kHz cut-off frequency, Butterworth Bandpass Filter with 150 kHz center frequency, Butterworth Bandpass Filter with 300 kHz center frequency, Chebyshev Low-Pass Filter with 150 kHz cut-off frequency and Chebyshev Low-Pass Filter with 300 kHz cut-off frequency. In order to create these responses, a generic Ackerberg-Mossberg biquad topology is used. Selection of the filter response is achieved by means of several customized 8-to-1 multiplexer circuit which consist of three stages of 2-to-1 multiplexers. In addition to the biquad design, we also performed design choices for the opamp that is used several times in the design.

**Index Terms**—Butterworth Filter, Chebyshev Filter, Low-pass Filter, Bandpass Filter, Multiplexer, Operational Amplifier Design

### I. INTRODUCTION

THIS article is prepared as a final report for the design project of the course “E4215 – Analog Filter Synthesis/Design” at Columbia University in the City of New York. Second section explains how the transfer function of each filter response is obtained along with the MATLAB plots of each filter response. Third section describes the procedure for implementing the transfer function. Fourth section demonstrates all subcomponents of the filter including the operational amplifier and design decisions taken while determining the op-amp parameters. Fifth section depicts the schematics of each filter. The last section gives the results of the simulations run to verify the functionality of the programmable anti-aliasing analog filter.

Submitted on 12/18/2020 as a report for the final design project of the E4215 at Columbia University in the City of New York by:

Liping Hu, [lh3009@columbia.edu](mailto:lh3009@columbia.edu)  
Sinan Yilmaz, [sy2943@columbia.edu](mailto:sy2943@columbia.edu)

### II. FILTER TRANSFER FUNCTION

Figure 1 to 3 illustrate Butterworth low-pass response. Figure 4 to 6 illustrate Butterworth band-pass filter response. Figure 7 to 9 illustrate Chebyshev low-pass filter response.

$N = 6 = \frac{\log \left[ \frac{10 \text{ dB} - 1}{10 \text{ dB} - 1} \right]}{2 \log \left( \frac{w_o}{w_p} \right)}$	$N = 6; \quad \varphi_1 = \frac{\pi}{12}, \quad \varphi_2 = \frac{3\pi}{12}, \quad \varphi_3 = \frac{5\pi}{12},$ $\varphi_4 = \frac{7\pi}{12}, \quad \varphi_5 = \frac{9\pi}{12}, \quad \varphi_6 = \frac{11\pi}{12},$
$P_1 = w_o \Sigma - \sin \left( \frac{\pi}{12} \right) - j \cos \left( \frac{\pi}{12} \right)$	$P_4 = w_o \Sigma - 0.9659 + j 0.258819$
$= w_o \Sigma - 0.2588 - j 0.9659$	$P_5 = w_o \Sigma - 0.7071 + j 0.7071$
$P_2 = w_o \Sigma - \sin \left( \frac{3\pi}{12} \right) - j \cos \left( \frac{3\pi}{12} \right)$	$P_6 = w_o \Sigma - 0.2588 + j 0.9659$
$= w_o \Sigma - 0.7071 - j 0.7071$	$Q_{1,6} = \frac{1}{2 \times 0.258819} = 1.93 = Q_1$
$P_3 = w_o \Sigma - \sin \left( \frac{5\pi}{12} \right) - j \cos \left( \frac{5\pi}{12} \right)$	$Q_{2,5} = \frac{1}{2 \times 0.7071} = 0.707 = Q_2$
$= w_o \Sigma - 0.9659 - j 0.2588$	$Q_{3,4} = \frac{1}{2 \times 0.965926} = 0.518 = Q_3$

$$H(s) = \frac{w_o^6}{(s^2 + 0.518 w_o s + w_o^2)(s^2 + j \sqrt{w_o} w_o s + w_o^2)(s^2 + 1.93 w_o s + w_o^2)}$$

Fig. 1. Calculations for the Butterworth low-pass filter transfer function.

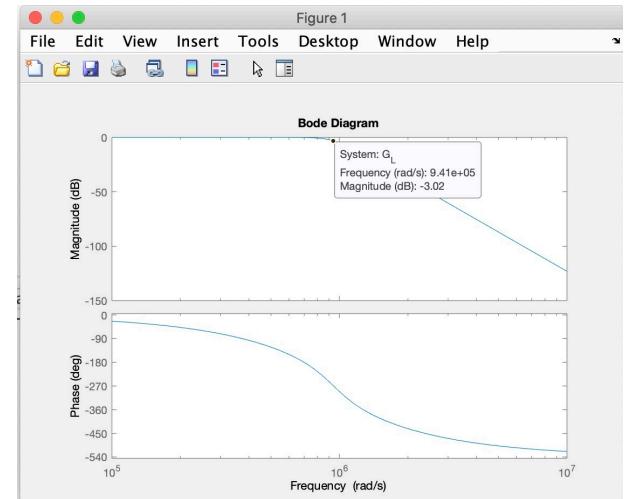


Fig. 2. MATLAB plots of the Butterworth low-pass filter response with a 150 kHz cut-off frequency. The 3dB frequency simulated is 9.41e+05 rad/s = 149.7KHz = 150KHz. The DC gain is 1v/v.

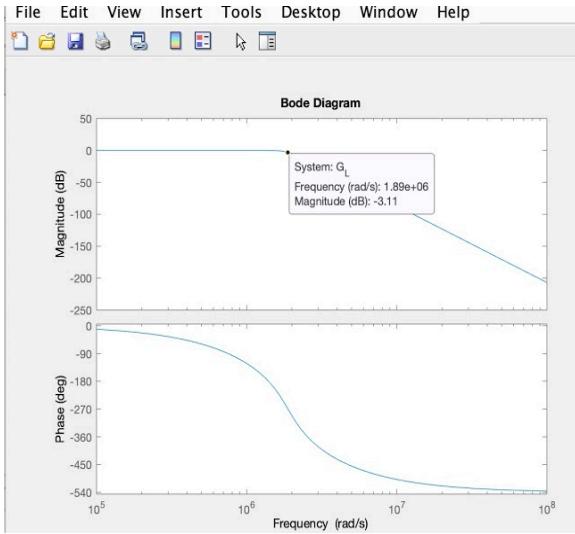


Fig. 3. MATLAB plots of the Butterworth low-pass filter response with a 300 KHz cutoff frequency. The 3dB frequency simulated is 1.89e+06 rad/s = 300KHz. The DC gain is 1v/v.

$$\begin{aligned}
 \omega_0 &= 2\pi \times 150 \text{ Krad/s} = 942478 = 0.94 \times 10^6 \text{ rad/s} = \omega_0 \Rightarrow R_A = 10.610 \\
 K_H &= 0 \rightarrow C_1 = 0F \\
 K_B &= 1 \rightarrow R_1 = R_B \\
 K_L &= 0 \rightarrow R_2 = 0 \\
 H(s) &= \frac{\omega_0}{Q_1 s + \omega_0} \cdot \frac{\omega_0}{Q_2 s + \omega_0} \cdot \frac{\omega_0}{Q_3 s + \omega_0} \\
 H(s) &= \frac{\omega_0^3}{(Q_1 Q_2 Q_3) s^3} \\
 H(s) &= \frac{\omega_0^3}{(s^2 + s \frac{\omega_0}{Q_1} + \omega_0^2)(s^2 + s \frac{\omega_0}{Q_2} + \omega_0^2)(s^2 + s \frac{\omega_0}{Q_3} + \omega_0^2)}
 \end{aligned}$$

Fig. 4. Calculations for the Butterworth band-pass filter transfer function.

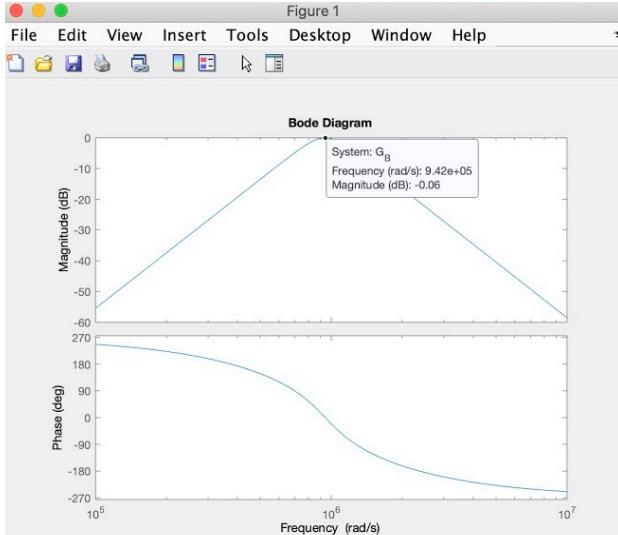


Fig. 5. MATLAB plots of the Butterworth band-pass filter response with a 150 KHz cutoff frequency. The center frequency is 9.42e+05 rad/s = 149.9KHz = 150KHz. The DC gain is 1v/v.

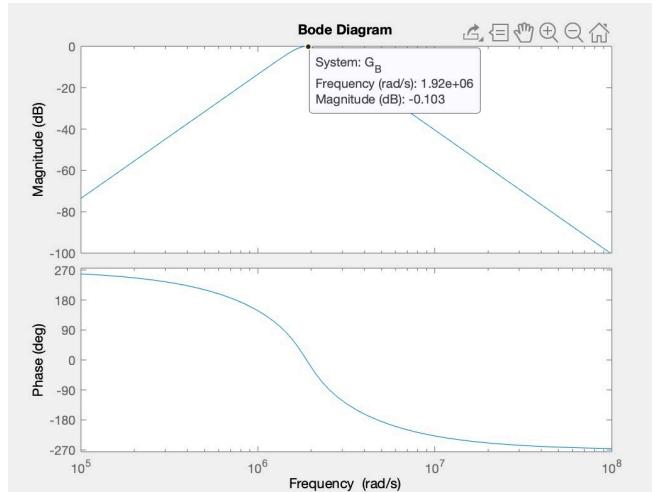


Fig. 6. MATLAB plots of the Butterworth band-pass filter response with a 300 KHz cutoff frequency. The center frequency is 1.92e+06 rad/s = 300KHz. The DC gain is 1v/v.

$$\begin{aligned}
 \text{For Chebyshev } LPF: f_l = 150 \text{ kHz}, f_h = 300 \text{ kHz}, K_B = 0.06 / 1v; N = 6; \alpha_{max} = 2dB \\
 w_p = \omega_0 \\
 \omega_0 = 942478 \text{ rad/s}, \quad w_h = 1.884956 \text{ rad/s} \\
 \zeta = \sqrt{10^{2m+1}-1} = \sqrt{10^{3/10}-1} = 0.9976 \\
 Q = \frac{1}{N} \sinh^{-1}\left(\frac{1}{\zeta}\right) = \frac{1}{6} \sinh^{-1}\left(\frac{1}{0.9976}\right) = 0.14776 \\
 \gamma_1 = \frac{\pi}{12}, \quad \gamma_2 = \frac{3\pi}{12}, \quad \gamma_3 = \frac{5\pi}{12}, \quad \gamma_4 = \frac{7\pi}{12}, \quad \gamma_5 = \frac{9\pi}{12}, \quad \gamma_6 = \frac{11\pi}{12} \\
 P_1 = -w_p [\sinh(0.14776) \sin(\frac{\pi}{12}) + j \cosh(0.14776) \cos(\frac{\pi}{12})] \\
 P_1 = -w_p [0.03823 + j 0.976406] \\
 \omega_{n,1} = w_p \sqrt{0.03823^2 + 0.976406^2} = 92.0946 \text{ rad/s} = \omega_{n,1} = 0.977 w_p \quad \omega_n = 1884956 \times 0.977 \\
 \omega_1 = \frac{0.977 w_p}{2 \times 0.03823 \times w_p} = 12.78 = Q_1 \quad Q_1' = 12.78 \\
 P_2 = -w_p [\sinh(0.14776) \sin(\frac{3\pi}{12}) + j \cosh(0.14776) \cos(\frac{3\pi}{12})] \\
 = -w_p [0.104445 + j 0.714779] \\
 = -w_p \times 0.722369 = 68.0817 \text{ rad/s} = \omega_{n,2} \quad \omega_n = 1361633 \text{ rad/s} \\
 Q_2 = \frac{0.722369 w_p}{2 \times 0.104445 \times w_p} = 2.46 = Q_2 \quad Q_2' = 2.46 \\
 P_3 = -w_p [\sinh(0.14776) \sin(\frac{5\pi}{12}) + j \cosh(0.14776) \cos(\frac{5\pi}{12})] \\
 = -w_p [0.142674 + j 0.21627] \\
 = -w_p \times 0.298 = 28.0860 \text{ rad/s} = \omega_{n,3} \quad \omega_n = 561717 \text{ rad/s} \\
 Q_3 = \frac{0.298}{2 \times 0.142674} = 1.04 = Q_3 \quad Q_3' = 1.04 \\
 H(s) = \frac{w_p^6}{0.9916x2\zeta(s^2 + \frac{\omega_{n,1}^2}{12.78} + \omega_{n,1}^2)(s^2 + \frac{\omega_{n,2}^2}{2.46} + \omega_{n,2}^2)(s^2 + \frac{\omega_{n,3}^2}{1.04} + \omega_{n,3}^2)}
 \end{aligned}$$

Fig. 7. Calculations for the Chebyshev low-pass filter transfer functions. The blue marked symbols represent corresponding values for 300KHz cutoff frequency.

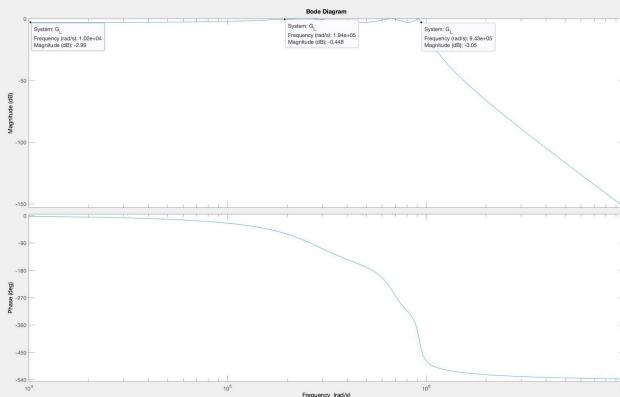


Fig. 8. MATLAB plots of the Chebyshev low-pass filter response with a 150 kHz cutoff frequency. The 3dB frequency simulated is  $9.43 \times 10^5$  rad/s = 150KHz. The DC gain is 1v/v.

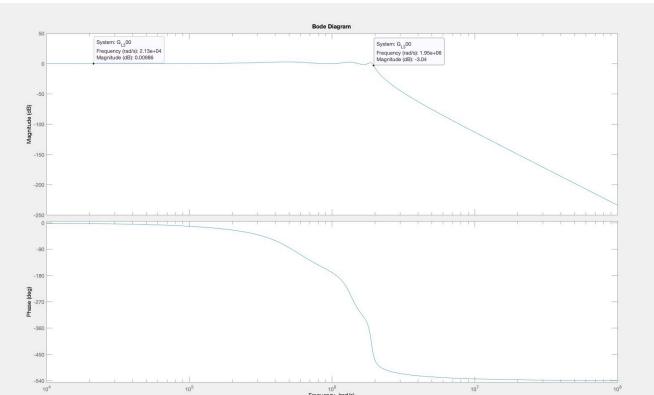


Fig. 9. MATLAB plots of the Chebyshev low-pass filter response with a 300 kHz cutoff frequency. The 3dB frequency simulated is  $1.95 \times 10^6$  rad/s = 310KHz. The DC gain is 1v/v.

### III. PROCEDURE FOR IMPLEMENTING TRANSFER FUNCTION.

$$\begin{aligned} f_0 &= 150 \text{ kHz}, \quad w_0 = 1.88496 \times 10^6 \text{ rad/s} = \frac{1}{R_A C_A}, \quad C_A = 100 \text{ pF} = 10^{-10} \text{ F} \\ R_A &= \frac{1}{w_0 C_A} = \frac{1}{1.88496 \times 10^6 \times 10^{-10}} = 530.5 \Omega \\ k_H = 0 &\rightarrow C_1 = 0 \text{ F} \quad Q_1 = 1.93 = \frac{R_B}{R_A} \Rightarrow R_B = 1.93 \times R_A = 1023.9 \Omega \\ k_B = 0 &\rightarrow R_1 = \infty \quad Q_2 = 0.707 = \frac{R_B}{R_{B2}}, \quad R_{B2} = 0.707 \times 530.5 \Omega = 375.1 \Omega \\ k_L = 1 &\rightarrow R_2 = R_1 = 530.5 \quad Q_3 = 0.518 \Rightarrow R_{B3} = 0.518 \times 530.5 \Omega = 274.8 \Omega \end{aligned}$$

$$\begin{aligned} f_0 &= 150 \text{ kHz} \quad w_0 = 2\pi f_0 \quad w_0 = 2\pi \times 150 \text{ kHz/s} = \frac{1}{R_A C_0} = 942478 \\ \text{assume } C_0 &= 100 \text{ pF} \quad R_0 = \frac{1}{w_0 C_0} = 1061.0 \Omega = R_B \\ k_H = 0 &= \left| -\frac{C_1}{C_0} \right| \quad \therefore C_1 = 0 \text{ F} \quad (\text{open circuit}) \\ k_B = 0 &= \left| -\frac{R_B}{R_A} \right| \quad \therefore R_1 = \infty \quad (\text{open circuit}) \\ k_L = 1 &= \left| -\frac{R_2}{R_A} \right| \quad \therefore R_A' = R_A = R_2 = 1061.0 \Omega \\ Q_1 = 1.93 &= \frac{R_B}{R_A} \Rightarrow R_B = R_A \times 1.93 = 1061.0 \Omega \times 1.93 = 2047.8 \Omega = R_{B1} \\ Q_2 = 0.707 &= \frac{R_B}{R_{B2}} \Rightarrow R_{B2} = R_A \times 0.707 = 1061.0 \times 0.707 = 750.1 \Omega = R_{B2} \\ Q_3 = 0.518 &= \Rightarrow R_{B3} = 549.6 \Omega = R_{B3} \end{aligned}$$

Fig. 10. calculation procedure for determining the resistor and capacitor values for the 6<sup>th</sup> order low-pass Butterworth filter in terms of cutoff frequency.

$$\begin{aligned} f_0 &= 150 \text{ kHz} \\ w_0 &= 2\pi \times 150 \text{ kHz/s} = 942478 = 0.94 \times 10^6 \text{ rad/s} = w_0 \Rightarrow R_A = 1061.0 \Omega \\ k_H = 0 &\rightarrow C_1 = 0 \text{ F} \\ k_B = 1 &\rightarrow R_1 = R_{B1} \\ k_L = 0 &\rightarrow R_2 = \infty \Omega \\ Q_1 = 1.93 &= \frac{R_B}{R_A} \Rightarrow R_B = R_A \times 1.93 = 1061.0 \Omega \times 1.93 = 2047.8 \Omega = R_{B1} \\ Q_2 = 0.707 &= \frac{R_B}{R_{B2}} \Rightarrow R_{B2} = R_A \times 0.707 = 1061.0 \times 0.707 = 750.1 \Omega = R_{B2} \\ Q_3 = 0.518 &= \Rightarrow R_{B3} = 549.6 \Omega = R_{B3} \end{aligned}$$

$$\begin{aligned} f_0 &= 300 \text{ kHz} \\ w_0 &= \frac{1}{R_A C_A}, \quad C_A = 100 \text{ pF} = 10^{-10} \text{ F} \\ R_A &= \frac{1}{w_0 C_A} = \frac{1}{1.88496 \times 10^6 \times 10^{-10}} = 530.5 \Omega \\ k_H = 0 &\rightarrow C_1 = 0 \text{ F} \quad Q_1 = 1.93 = \frac{R_B}{R_A} \Rightarrow R_B = 1.93 \times R_A = 1023.9 \Omega \\ k_B = 1 &\rightarrow R_1 = R_{B1} \quad Q_2 = 0.707 = \frac{R_B}{R_{B2}}, \quad R_{B2} = 0.707 \times 530.5 \Omega = 375.1 \Omega \\ k_L = 0 &\rightarrow R_2 = \infty \Omega \quad Q_3 = 0.518 \Rightarrow R_{B3} = 0.518 \times 530.5 \Omega = 274.8 \Omega \end{aligned}$$

Fig. 11. calculation procedure for determining the resistor and capacitor values for the 6<sup>th</sup> order band-pass Butterworth filter in terms of cutoff frequency.

$$\begin{aligned} f_0 &= 150 \text{ kHz} \\ \text{let } C_A &= 100 \text{ pF} = 10^{-10} \text{ F} \\ k_L = 1 &= \left| -\frac{R_A'}{R_2} \right| \Rightarrow R_A' = R_A = R_2 \\ w_{B1} &= \frac{1}{R_A C_A} = 920946 \text{ rad/s}; \quad R_{A1} = \frac{1}{w_{B1} \times C_A} = 1085.8 \Omega \\ Q_1 = \frac{R_B}{R_{A1}} &= 12.78 \quad \therefore R_{B1} = 12.78 \times 1085.8 \Omega = 138770 \Omega \\ w_{B2} &= 610817 \Rightarrow R_{A2} = \frac{1}{w_{B2} \times C_A} = 14489.9 \Omega \\ Q_2 = 3.46 &= \Rightarrow R_{B2} = 3.46 \times 2938 = 50822.5 \Omega = R_{B2} \\ w_{B3} &= 280860 \Rightarrow R_{A3} = 35605.5 \Omega \\ Q_3 = 1.04 &= \Rightarrow R_{B3} = 37029 \Omega \end{aligned}$$

$$\begin{aligned} \text{For chebyshev } 4\text{PF: } f_0 &= 300 \text{ kHz} \\ w_0 &= 1.884956 \text{ rad/s} \quad C_A = 100 \text{ pF} = 10^{-10} \text{ F} \\ w_{B1} &= 1841602 \text{ rad/s} \quad R_{B1} = Q_1 \times R_{A1} = 69396 \Omega \\ w_{B2} &= 1361633 \text{ rad/s} \quad k_H = 0 \Rightarrow C_1 = 0 \\ w_{B3} &= 56717 \text{ rad/s} \quad k_B = 0 \Rightarrow R_1 = \infty \Omega \\ R_{A1} &= \frac{1}{w_{B1} C_A} = 543.0 \Omega \quad R_{B1} = Q_1 \times R_{A1} = 69396 \Omega \\ R_{A2} &= \frac{1}{w_{B2} C_A} = 7344 \Omega \quad R_{B2} = Q_2 \times R_{A2} = 25411 \Omega \\ 2 \Rightarrow &= \frac{1}{w_{B3} C_A} = 17803.2 \quad R_{B3} = Q_3 \times R_{A3} = 18515 \Omega \end{aligned}$$

Fig. 12. calculation procedure for determining the resistor and capacitor values for the 6<sup>th</sup> order low-pass Chebyshev filter in terms of cutoff frequency.

TABLE 1.

Resistor and capacitor values for the programmable anti-aliasing filter design.

	Butterworth			Chebyshev		
	wo1	Q1	wo2	Q2	wo3	Q3
150KHz	920946	12.78	680817	3.46	280860	1.04
	CA	100pF	100pF	100pF	100pF	100pF
	C1	none	none	none	none	none
	R1	none	none	none	none	none
	R2	10610 Ohm	10610 Ohm	10610 Ohm	10858	14689
	RA-RA'	10610 Ohm	10610 Ohm	10610 Ohm	RA	10858
300KHz	RB	20478 Ohm	7501 Ohm	5496 Ohm	RB	138770
	wo:	942477.78				
	CA	100pF	100pF	100pF	100pF	100pF
	C1	not there	not there	not there	none	none
	R1	5305	5305	5305	R2	5430
	RA-RA'	5305	5305	5305	RA	5430
BPF:	RB	10239	3751	2748	RB	69396
	wo:	1884955.6				
	CA	100pF	100pF	100pF	100pF	100pF
	C1	not there	not there	not there	none	none
	R1	20478 Ohm	7501 Ohm	5496 Ohm	RA	10858
	RA-RA'	10610 Ohm	10610 Ohm	10610 Ohm	RB	138770

#### IV. SUBCOMPONENTS

##### A. Analog Multiplexers

Analog multiplexers are needed in our design to select the wanted filter response. We have utilized the 2-to-1 multiplexer topology given in the course. (Fig. 13)

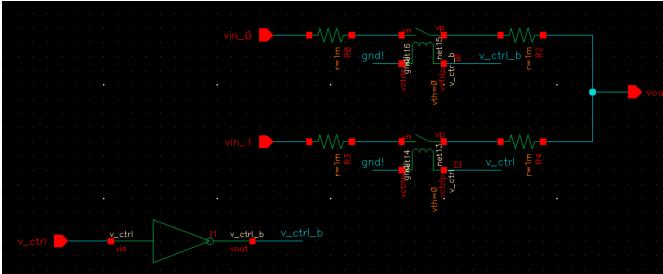


Fig. 13. 2-to-1 MUX

This multiplexer design has been cascaded to create an 8-to-1 MUX. (Fig. 14) This 8-to-1 MUX is used to choose the resistor values necessary for particular filter response. An example of this selection is provided in Fig. 15.

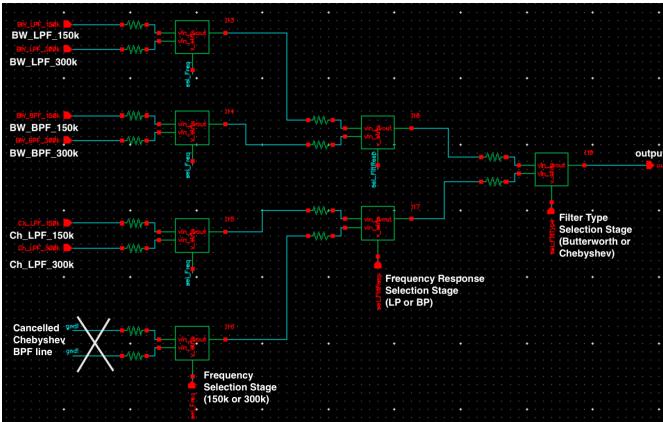


Fig. 14: 8-to-1 MUX

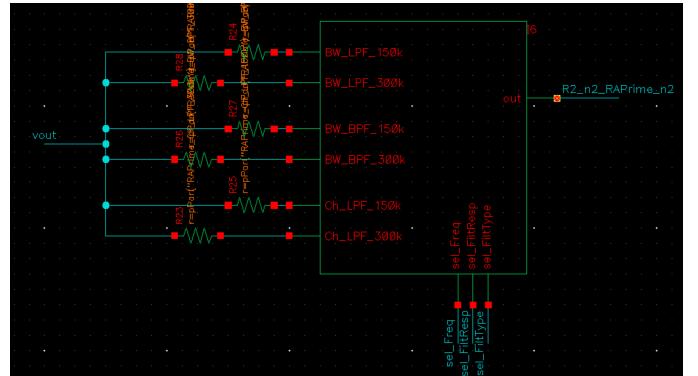


Fig. 15. An example of resistors multiplexed by using the 8-to-1 MUX

##### B. Operational Amplifier

A simple operational amplifier model is designed for our system. In order to meet the specifications given in the project description, we determined the  $g_m$ ,  $I_{o,\max}$ ,  $R_{in}$ ,  $C_1$ ,  $A_2$ , Output swing and  $R_{out}$ .

We started the analysis with  $g_m$  calculation, assuming  $C_1 = 50$  pF. Unity gain frequency formula  $w_t = g_m/C_1$  is used to calculate a rough estimate for the  $g_m$ . In order for  $w_t$  to not interfere with the passband of the filter, we should have  $g_m$  in the order of mS.

After determining the rough estimate, a parametric sweep is performed to fine tune the  $g_m$ . This parametric sweep is used to determine a value while considering the trade-off between better frequency response and low power consumption since  $g_m$  is affecting both parameters. Fig. 16 shows us this trade-off when  $g_m$  is swept between 1 mS and 10 mS.

Fig. 16: Parametric Analysis to determine  $g_m$ 

Above figure includes power consumption estimates by using the  $I_{o,\max}$  value that is calculated by using the specification  $I_{o,\max}/g_m = 200$  mV.

$$g_m = 4 \text{ mS}$$

$$I_{o,\max} = \pm 800 \mu\text{A}$$

In addition to these specifications, we should calculate the DC gain of our opamp along with other parameters:

$$\text{DC Gain} = A_2 * g_m * R = 104 \text{ dB}$$

$$f_p = \frac{1}{R C_1 A_2 * 2\pi} = 500 \text{ Hz}$$

Since our opamp has a single pole, there will be a 20 dB/dec slope during the degrade of the gain while frequency increases. At 500 kHz, we would still have a 44 dB gain for the opamp which will not interfere with the operation of our programmable filter.

$$f_t = \frac{g_m}{C_1} = 80 \text{ MHz}$$

The latest form of the opamp is demonstrated in Fig. 17.

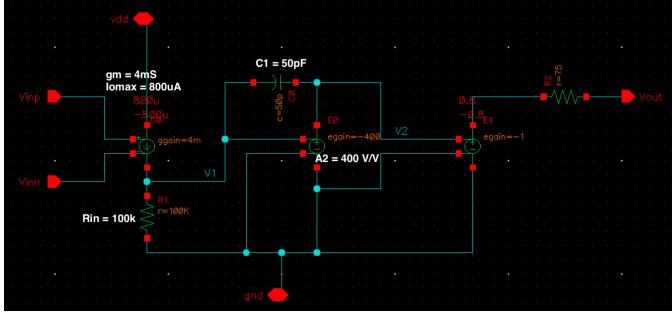


Fig. 17. Operational Amplifier Design

## V. SCHEMATICS

In our filter, we have utilized the generic Ackerberg-Mossberg biquad to create a second order response that can produce all filter responses. (Fig. 18)

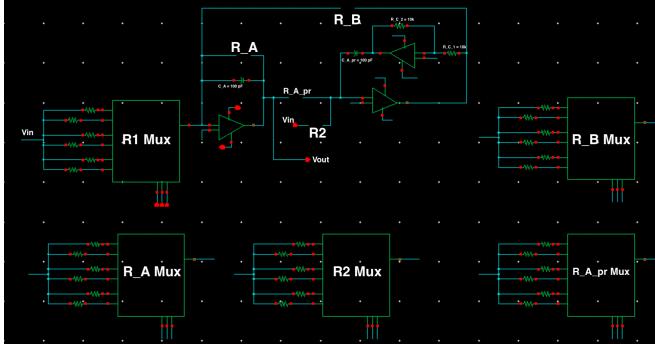


Fig. 18. Generic Ackerberg-Mossberg Biquad along with resistor multiplexing

Only some of the resistors are changing values from one design to another. Capacitors are chosen as 100 pF. Positive feedback loop's resistors are also fixed to 10 kΩ. For low-pass and bandpass response, most of the components are the same but some of the components are changing from one to another. Hence, since we're using only a single generic schematic, we performed the open-circuit as a 1 TΩ resistor value if that resistor is not used for that topology.

In order to create a sixth order filter response, three biquads are cascaded as shown in Fig. 19. The resistor values are entered as a pParameter and shown in this figure. To account for the resistor associated with the multiplexers, we used the resistor values 300Ω less than the ones calculated in our table.

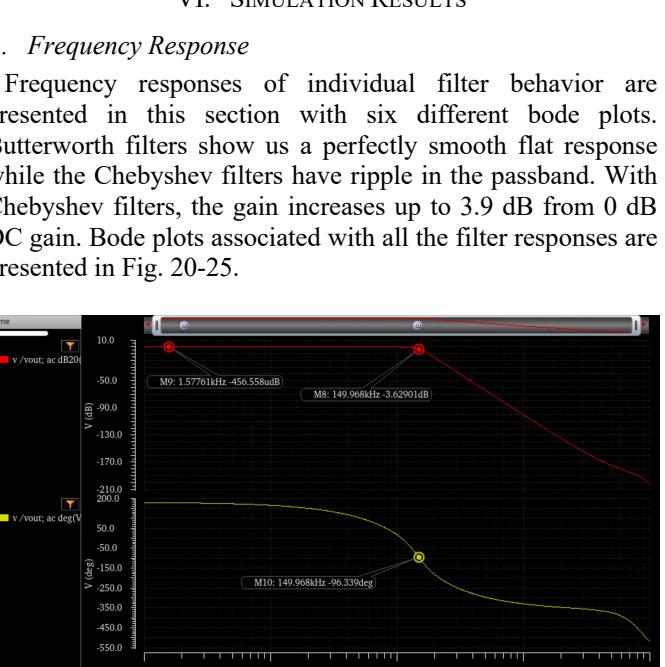
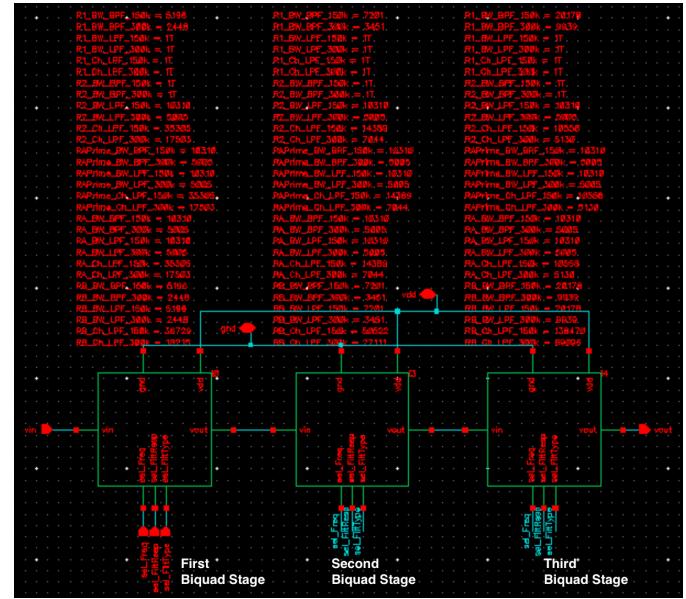


Fig. 20. Butterworth LPF with 150 kHz Cut-off Frequency

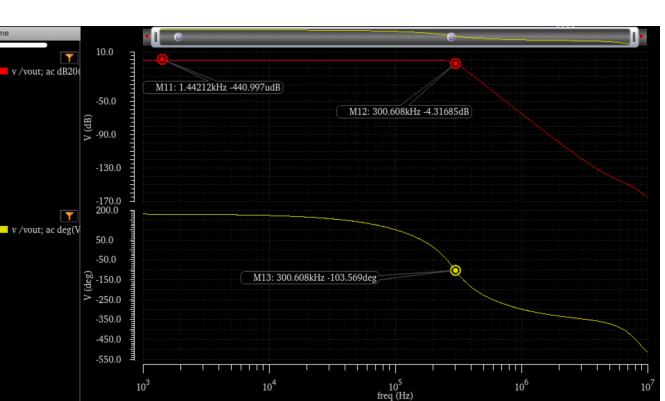


Fig. 21. Butterworth LPF with 300 kHz Cut-off Frequency

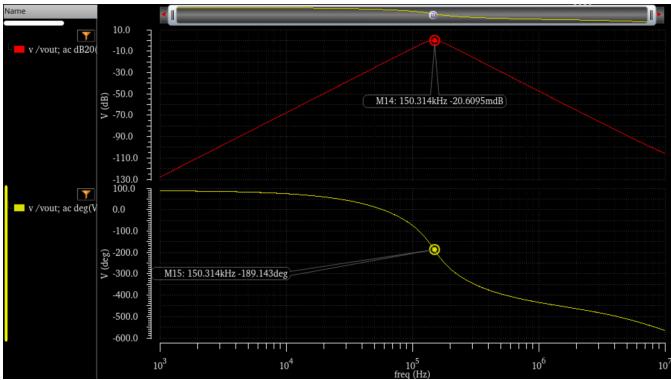


Fig. 22. Butterworth BPF with 150 kHz Center Frequency

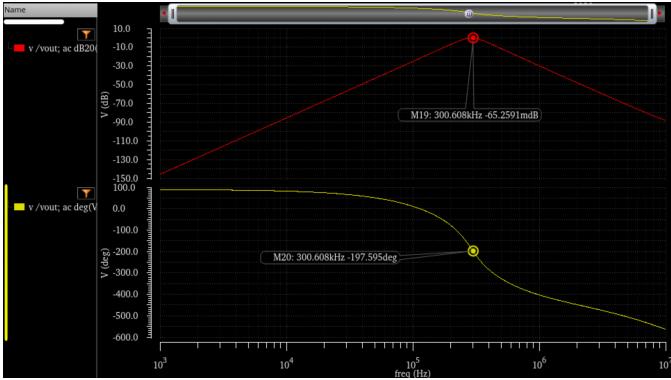


Fig. 23. Butterworth BPF with 300 kHz Center Frequency

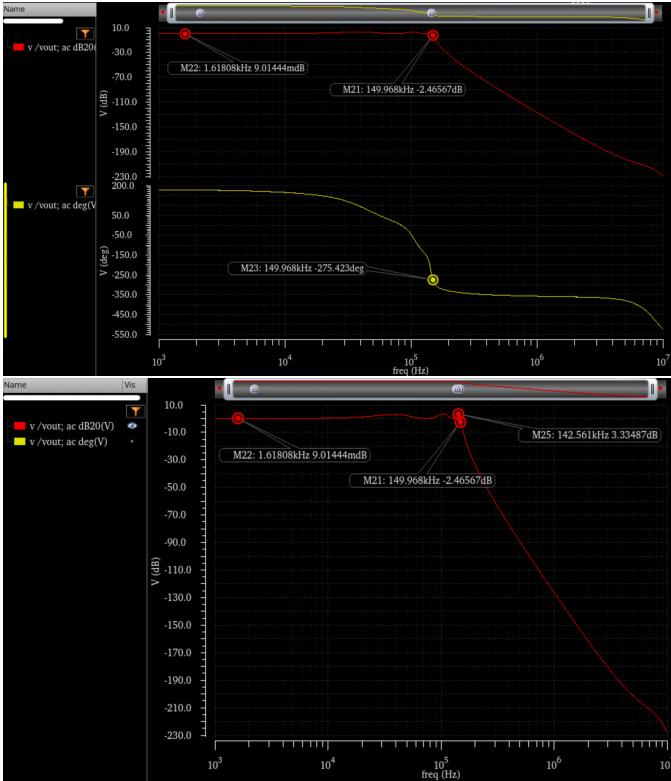


Fig. 24. Chebyshev LPF with 150 kHz Cut-off Frequency

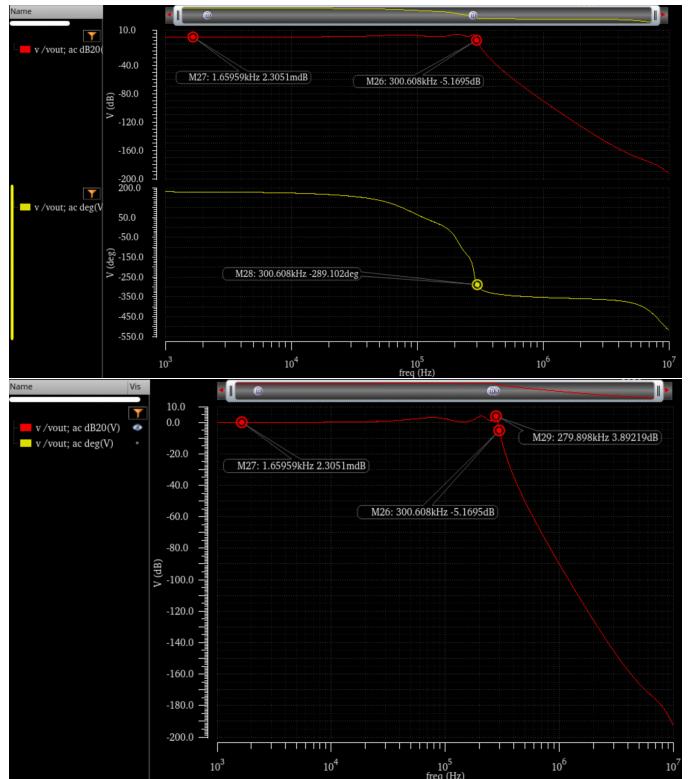


Fig. 25. Chebyshev LPF with 300 kHz Cut-off Frequency

### B. Transient Simulations to show adequate slew rate

Slew rate requirement for the opamp is calculated by using the highest frequency of operation (300 kHz) and output swing (0.8 V). This specification requires us to have a slew rate of 0.24 MV/s.

A transient analysis is performed on the opamp to prove that our design satisfies the slew rate requirement. For this analysis, a new test bench is created where the opamp is in voltage buffer mode and a pulse voltage source is applied at the input. (Fig. 26)

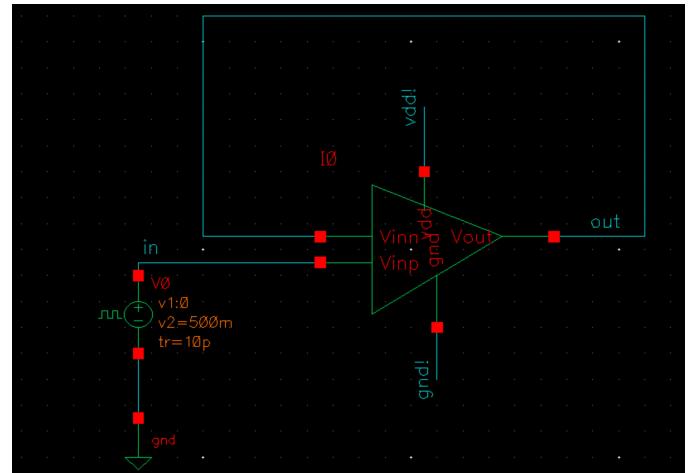


Fig. 26: Slew Rate transient analysis test bench

With this test bench, we expect to see that output will follow the input pulse waveform. However, because of the slew rate limitation that our design has, there will be a latency between

the input waveform and the output waveform. This has been shown in Fig. 27.



Fig. 27: Slew rate transient analysis waveforms

With this analysis, we see that we meet the slew rate requirement of 0.24 MV/s with a slew rate of 15.68 MV/s.

### C. Power Consumption

Power calculation is performed by using the simplified formula for our opamp topology.

$$Power_{SingleOpamp} = I_{o,max} * (V_{dd} - V_{ss}) * 3$$

$$Total\ Power = Power_{SingleOpamp} * 9$$

Supply voltage levels are given as:

$$V_{dd} = 1 \& V_{ss} = -1$$

Thus, the total power consumption of the 6<sup>th</sup> order filter is calculated as:

$$Total\ Power = 43.2\ mW$$

### D. Table for Figures of Merit

Parameter	Value
Opamp $g_m$	4 mS
Opamp $I_{o,max}$	800 $\mu A$
Opamp Slew Rate	15.68 MV/s
Opamp DC Gain	104 dB
Opamp $f_p$ & $f_t$	500 Hz & 80 MHz
Power Consumption	43.2 mW